

EE413  
Lab 005  
the Operational Amplifier

Jonas Sjöberg      Esther Hedlund

Data Performed:    26 November 2014  
Instructor: TODO

**Abstract**

”This lab is meant to show the practical use of the operational amplifier in analog circuit design. Several common circuit configurations will be discussed.”

## Contents

<b>1</b>	<b>Circuit prototyping setup</b>	<b>2</b>
<b>2</b>	<b>Inverting DC Amplifier</b>	<b>2</b>
2.1	Theory . . . . .	2
2.2	Measurements . . . . .	3
<b>3</b>	<b>Inverting AC Amplifier</b>	<b>3</b>
3.1	Oscilloscope shots . . . . .	3
3.2	Measurements . . . . .	3
<b>4</b>	<b>Non-inverting DC Amplifier</b>	<b>4</b>
4.1	Measurements . . . . .	4
<b>5</b>	<b>Non-inverting AC Amplifier</b>	<b>4</b>
5.1	Measurements . . . . .	4
<b>6</b>	<b>Active full wave rectifier</b>	<b>4</b>
<b>7</b>	<b>Results</b>	<b>6</b>

## 1 Circuit prototyping setup

The circuit was build on a solderless breadboard, using through-hole parts. A classic 741 op amp was used with a +/-15V power supply.

## 2 Inverting DC Amplifier

### 2.1 Theory

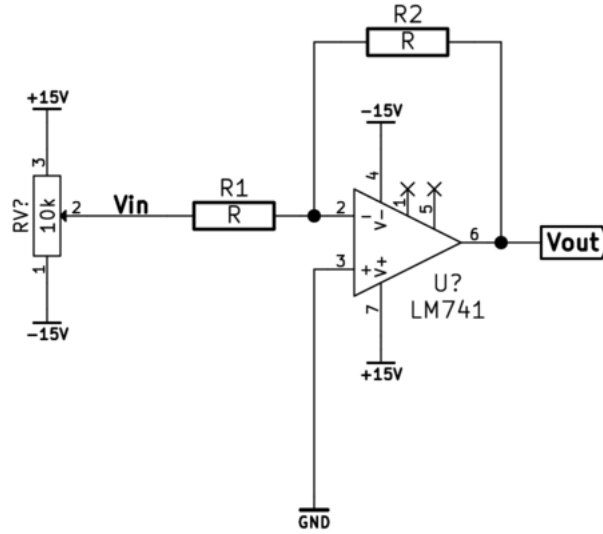


Figure 1: Inverting DC amplifier

The basic topology for an inverting amplifier is shown in Figure 1. Gain,  $A_v$ , can be expressed as a ratio of the feedback impedance to the input impedance. A fraction of the output is fed back, causing the op amp to compensate and in effect amplify.

$$A_v = \frac{R_2}{R_1} \quad (1)$$

The circuit gain for ideal components is therefore;  
For  $R_2 = 100k\Omega$ :

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \quad (2)$$

$$= \frac{100k\Omega}{10k\Omega} = 10 \quad (3)$$

$$= 20 \times \log \frac{10}{1} = 20dB \quad (4)$$

For  $R_2 = 10k\Omega$ :

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \quad (5)$$

$$= \frac{10k\Omega}{10k\Omega} = 10 \quad (6)$$

$$= 20 \times \log \frac{1}{1} = 0dB \quad (7)$$

In both cases, the signal phase is inverted  $180^\circ$ .

## 2.2 Measurements

Measured values for the test setup.

Uin (V)	Uout (V)	Av (ggr)
-0.105	+1.087	-10.54
-1.008	+10.236	-10.15
+1.004	-10.104	-10.06

Table 1:  $R_2 = 100k\Omega$

Uin (V)	Uout (V)	Av (ggr)
-0.1051	+0.1051	-1
-1.008	+1.008	-1
+1.004	-1.004	-1

Table 2:  $R_2 = 10k\Omega$

## 3 Inverting AC Amplifier

### 3.1 Oscilloscope shots

### 3.2 Measurements

Measured amplification = — Measured phase =  $180^\circ$  Theoretical amplifier =  
Theoretical phase =

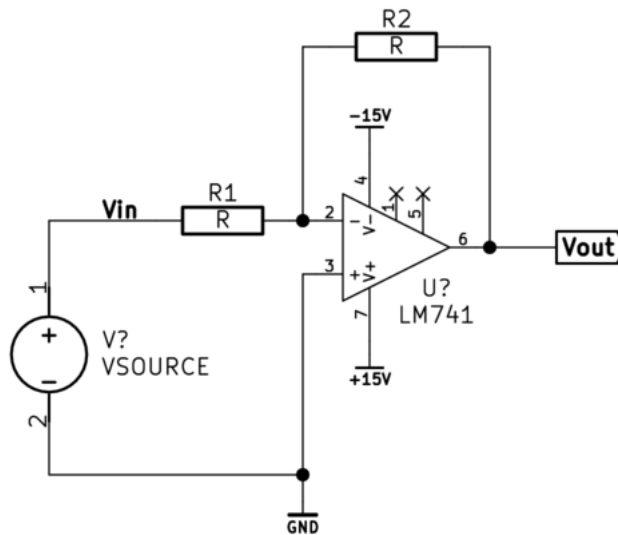


Figure 2: Inverting AC amplifier

## 4 Non-inverting DC Amplifier

$$A_v = 1 + R_2/R_1$$

### 4.1 Measurements

U <sub>in</sub> (V)	U <sub>out</sub> (V)	A <sub>v</sub> (ggr)
+0.1007	+0.2164 2	.15
+1.002	+2.048 2	.04
-1.005	-2.03 2	.019

Table 3: R<sub>2</sub> = 10kΩ

U <sub>in</sub> (V)	U <sub>out</sub> (V)	A <sub>v</sub> (ggr)
+0.1009	+1.178	11.67
+1.1013	+11.3	11.15
-1.004	-11.09	11.05

Table 4: R<sub>2</sub> = 100kΩ

## 5 Non-inverting AC Amplifier

### 5.1 Measurements

Input signal amplitude =

Output signal amplitude =

Measured amplification =

Measured phase =

Theoretical amplification = Theoretical phase =

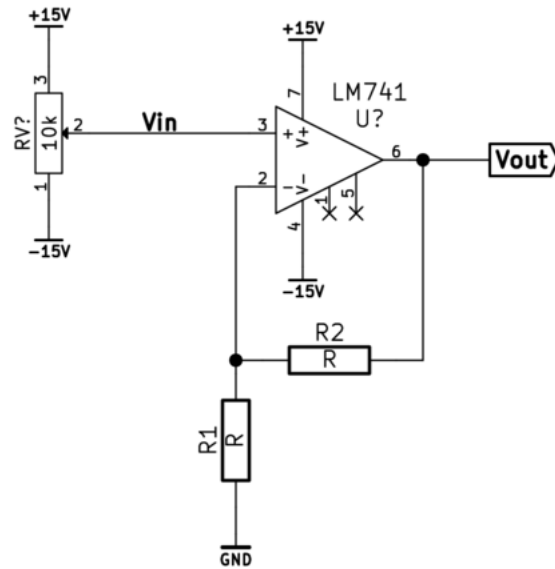


Figure 3: Non-inverting DC amplifier

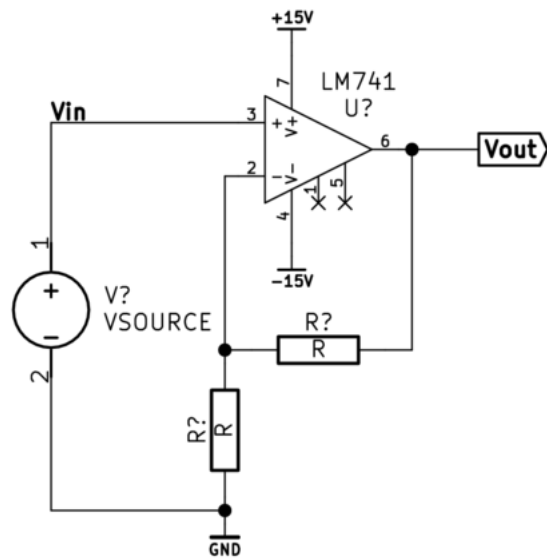


Figure 4: Non-inverting AC amplifier

recovery and rise time faster when D1 biases on. This improves circuit response times.

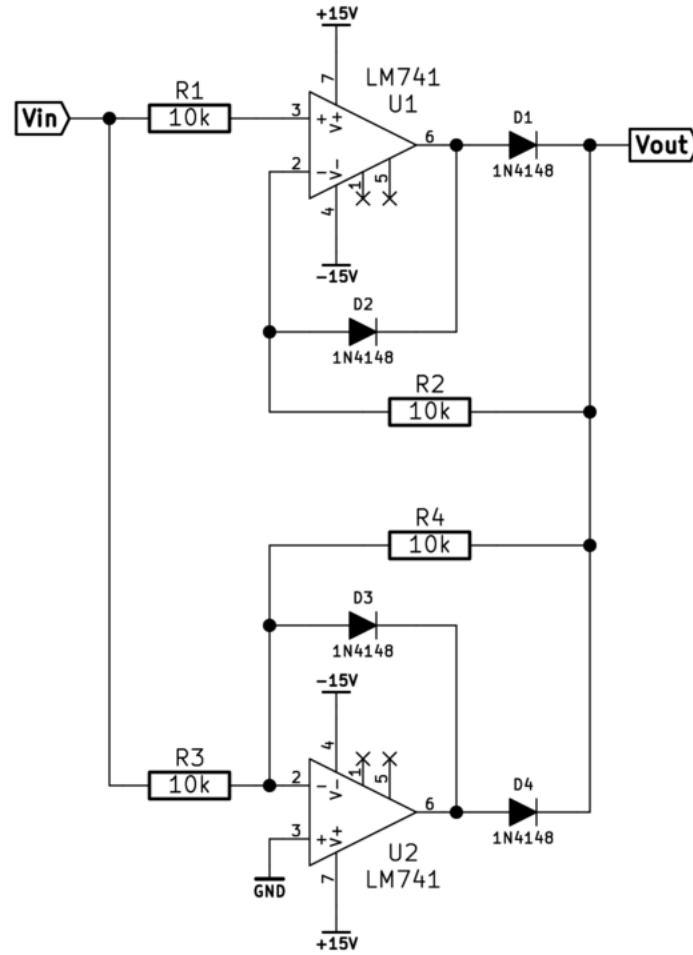


Figure 5: Active full wave rectifier

## 7 Results

TODO