

EE413  
Lab 005  
the Operational Amplifier

Jonas Sjöberg      Esther Hedlund

Data Performed:    26 November 2014  
Instructor: TODO

**Abstract**

”This lab is meant to show the practical use of the operational amplifier in analog circuit design. Several common circuit configurations will be discussed.”

# 1 Inverting DC Amplifier

## 1.1 Theory

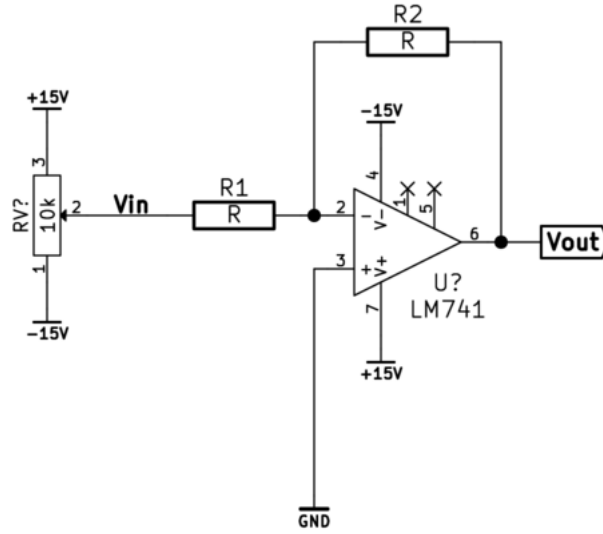


Figure 1: Inverting DC amplifier

The basic topology for an inverting amplifier is shown in 1. Gain,  $A_v$ , can be expressed as a ratio of the feedback impedance to the input impedance. A fraction of the output is fed back, causing the op amp to compensate and in effect amplify.

$$A_v = \frac{R_2}{R_1} \quad (1)$$

The circuit gain for ideal components is therefore;  
For  $R_2 = 100k\Omega$ :

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \quad (2)$$

$$= \frac{100k\Omega}{10k\Omega} = 10 \quad (3)$$

$$= 20 \times \log \frac{10}{1} = 20dB \quad (4)$$

For  $R_2 = 10k\Omega$ :

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \quad (5)$$

$$= \frac{10k\Omega}{10k\Omega} = 10 \quad (6)$$

$$= 20 \times \log \frac{1}{1} = 0dB \quad (7)$$

In both cases, the signal phase is inverted  $180^\circ$ .

## 1.2 Measurements

Uin (V)	Uout (V)	Av (ggr)
-0.105	+1.087	-10.54
-1.008	+10.236	-10.15
+1.004	-10.104	-10.06

Table 1:  $R_2 = 100k\Omega$

Uin (V)	Uout (V)	Av (ggr)
-0.1051	+0.1051	-1
-1.008	+1.008	-1
+1.004	-1.004	-1

Table 2:  $R_2 = 10k\Omega$

## 2 Inverting AC Amplifier

### 2.1 Oscilloscope shots

### 2.2 Measurements

Measured amplification = — Measured phase =  $180^\circ$  Theoretical amplification =  
Theoretical phase =

## 3 Non-inverting DC Amplifier

$$A_v = 1 + R_2/R_1$$

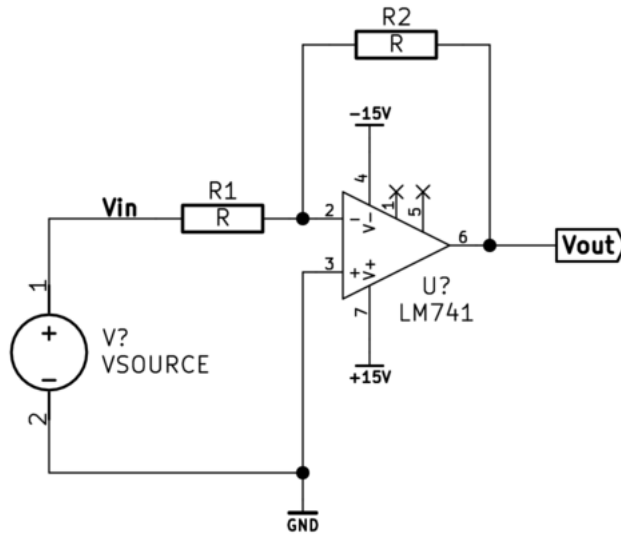


Figure 2: Inverting AC amplifier


### 3.1 Measurements

Uin (V)	Uout (V)	Av (ggr)
+0.1007	+0.2164 2	.15
+1.002	+2.048 2	.04
-1.005	-2.03 2	.019

Table 3:  $R2 = 10k\Omega$

Uin (V)	Uout (V)	Av (ggr)
+0.1009	+1.178	11.67
+1.1013	+11.3	11.15
-1.004	-11.09	11.05

Table 4:  $R2 = 100k\Omega$

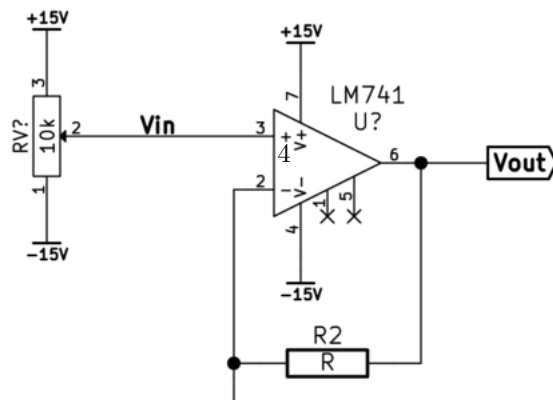

## 4 Non-inverting AC Amplifier

### 4.1 Measurements

Input signal amplitude =

Output signal amplitude =

Measured amplification =

Measured phase =

Theoretical amplification = Theoretical phase =

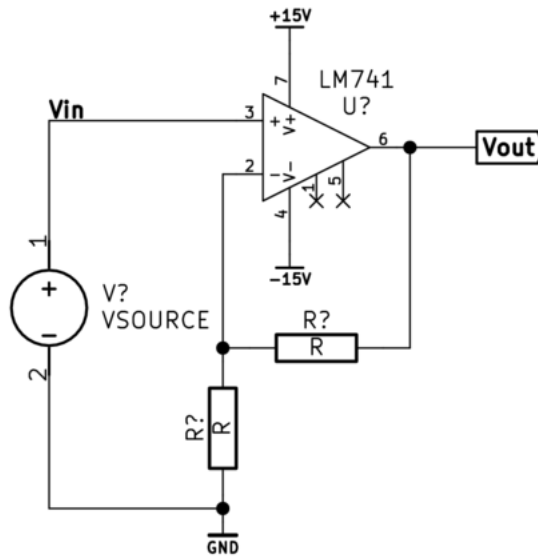


Figure 4: Non-inverting AC amplifier

## 5 Active full wave rectifier

Active rectifier does not suffer from the “deadzone” when the signal is too small to turn on the rectifying diode. The op amp compensates for the diode forward voltage drop. The circuit output is a full wave rectified version of the signal, with a frequency limit mostly set by the op amp bandwidth. Diode D2 prevents the op amp from hitting the rail hard when D1 is reverse biased. This makes the recovery and rise time faster when D1 biases on. This improves circuit response times.

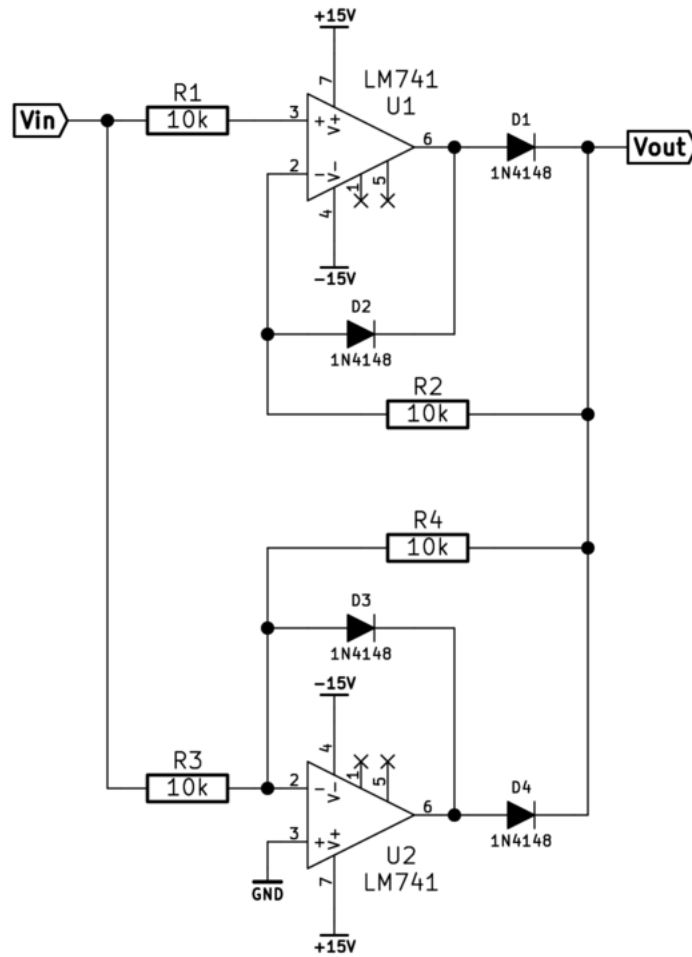


Figure 5: Active full wave rectifier